

# SCPY 394: Advanced Physics Laboratory II

## Lab 4: Lock-In Amplification

Dulyawat Boonvut, 6205110

October 25, 2022

### 1 Objective

To study basic Lock-In detection technique, working principle of Lock-In Amplifier, and its application.

### 2 Theories

The Lock-In detection technique is phase-sensitive detection; the signal component in phase with a reference signal is measured by using an input signal

$$V_{sig}(t) = V_{sig}^0 \sin(2\pi ft + \theta) \quad (1)$$

,same frequency  $f$  as the reference signal

$$V_{ref}(t) = V_{ref}^0 \sin(2\pi ft) \quad (2)$$

but with phase difference  $\theta$ .

For the Lock-In Amplifier used in the experiment, DSP Lock-In Amplifier Model SR830, the signal voltage is measured in in-phase component  $X(t) = V_{sig}^0 \cos(\theta)$  and quadrature component  $Y(t) = V_{sig}^0 \sin(\theta)$  with amplitude  $R(t) = \sqrt{X^2(t) + Y^2(t)} = V_{sig}^0$  and phase difference from the reference signal  $\theta = \arctan \frac{Y(t)}{X(t)}$

### 3 Capacitance measurement using Lock-In Amplifier

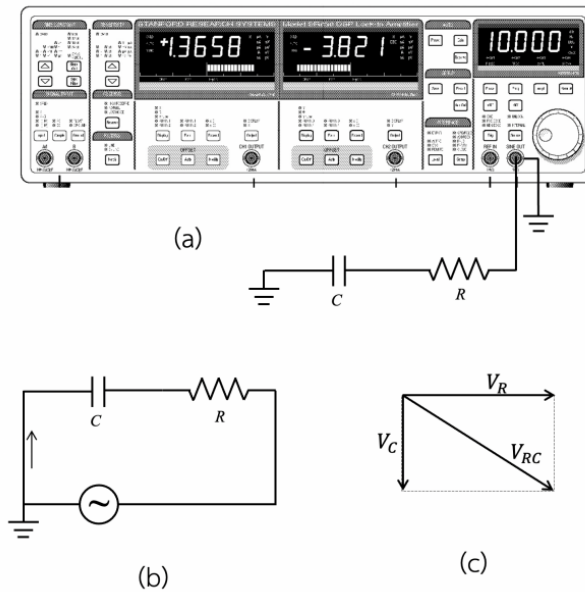


Figure 1: Circuit representation for using Lock-In Amplifier to measure capacitance

The sub-experiment is to measure capacitance by using the Lock-In Amplifier instead of an ordinary method using a multimeter. We connect a sine-wave source to an R-C circuit as shown in figure 1. The voltage between a capacitor is used as an input of the Lock-In Amplifier. The complete setup is shown in figure 2.



Figure 2: The experimental setup for using Lock-In Amplifier to measure capacitance

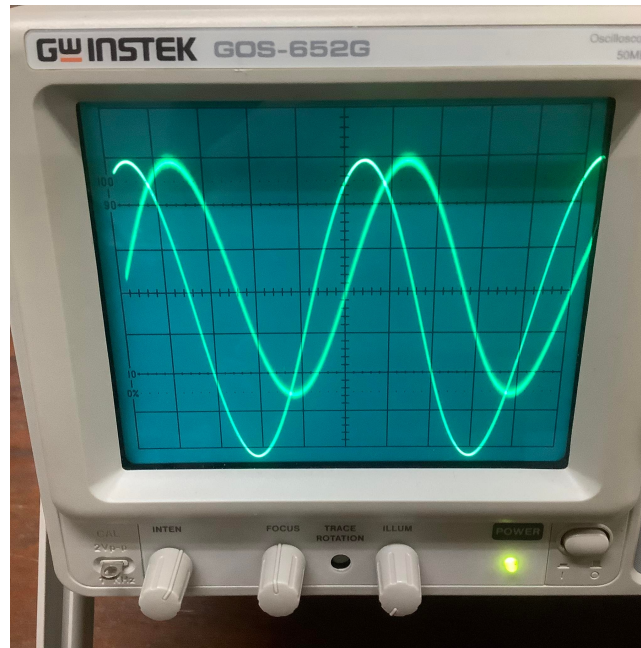


Figure 3: The result signals from the R-C circuit

From the setup, the result signals are shown in figure 3

From figure 1, measured quantities from the Lock-in Amplifier are shown in the below table.

Quantities from Lock-In Amplifier	Quantities from phasor diagram
$X$	voltage between capacitor $V_C$
$Y$	voltage between resistor $V_R$
$R$	source voltage $V_{RC}$
$\theta$	phase difference between $V_C$ and $V_{RC}$

Table 1: Comparison of quantities from Lock-In Amplifier and quantities from phasor diagram

Using a frequency range of 1 to 10 kHz, the obtained data is represented in the below graph.

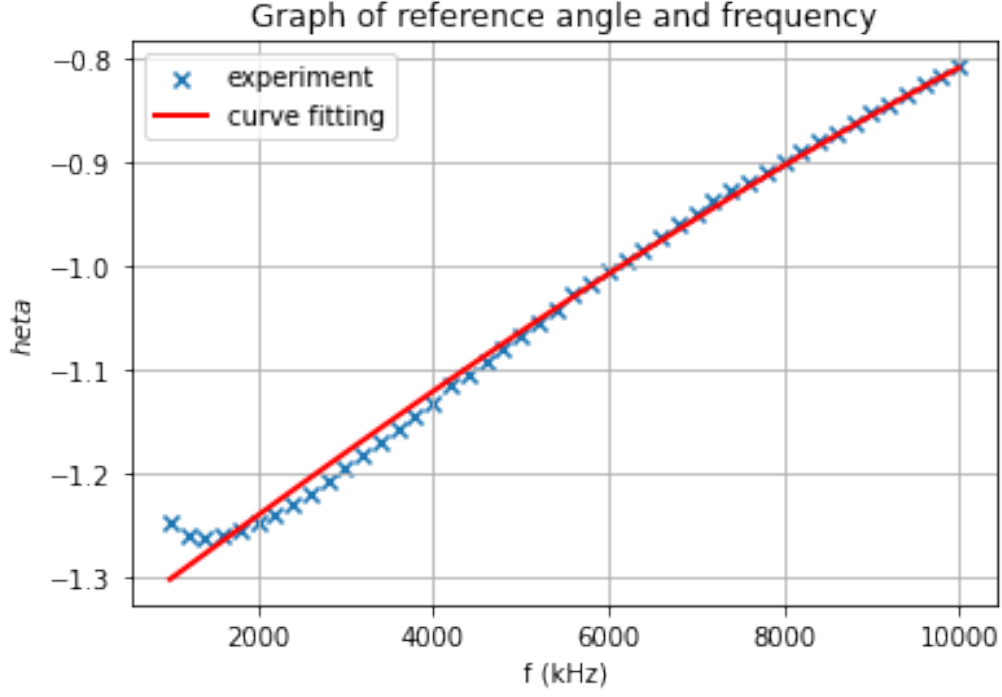


Figure 4: Graph of  $\theta$  and frequency of the R-C circuit

From the prior knowledge of AC circuits,  $\theta$  can be obtained from frequency.

$$\theta(f) = \arctan(2\pi RCf) + \theta_0 \quad (3)$$

where  $\theta_0$  is the reference phase, different for a unique system.

In the sub-experiment,  $R = 47 \, \Omega$ . With curve fitting, the capacitance is

$$C = 209 \pm 3 \, \text{nF}$$

## 4 Lock-In detection technique to measure noise-rich signal

The sub-experiment is to modulate the noise-rich signal. We compare using a multimeter with using a Lock-In Amplifier to examine both efficiencies.

### 4.1 Multimeter

We connect an electric source to a circuit (+5V). A non-zero output voltage, called **offset voltage**  $V_{\text{off}}$ , is expected even if electricity is unavailable in the system. In the sub-experiment, the offset voltage

$$V_{\text{off}} = 4.7 \pm 0.1 \, \text{mV} \quad (4)$$

Then the source is connected to the 2.0 V LED. From the observation, the voltage is  $251 \pm 1 \, \text{mV}$  and it increases from  $V_{\text{off}}$  for

$$V_0 - V_{\text{off}} = 246 \pm 1 \, \text{mV} \quad (5)$$

In the sub-experiment, a light-attenuated sheet is added to the system. The expected measured voltage must decrease when the number of sheets increases. For the number of sheets, the output voltage  $V_{\text{out}}$  is in the same order as the offset voltage, so the multimeter will be inapplicable.

From the sub-experiment, a graph of  $V_{\text{out}} = V - V_{\text{off}}$  with a different number of sheets is shown below.

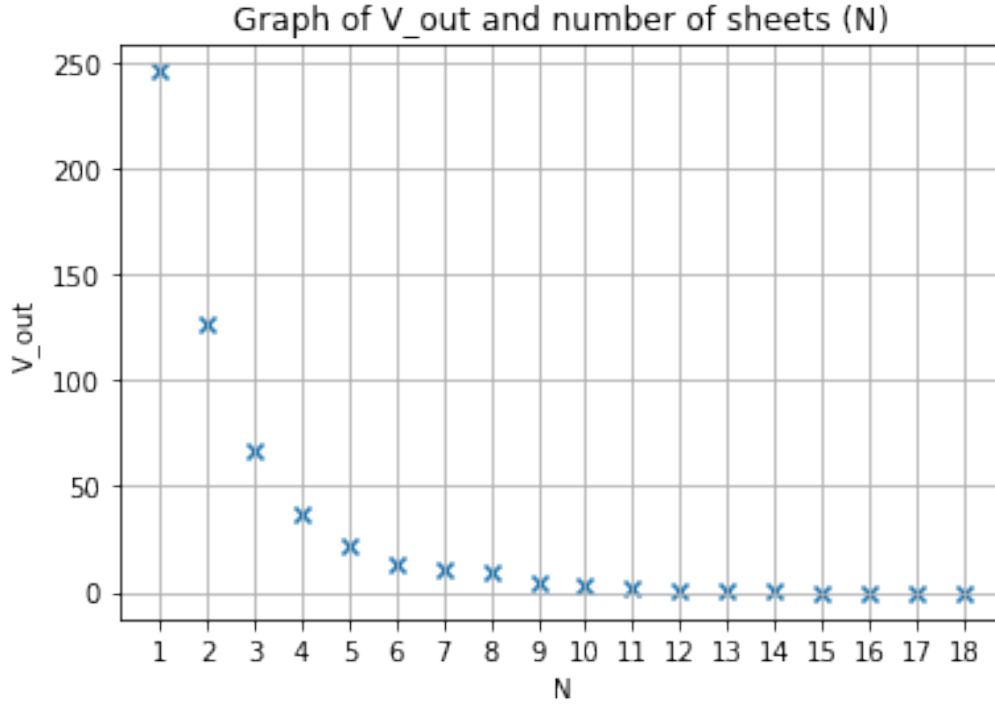


Figure 5: graph of  $V_{out}$  and number of sheets

From the graph 5, the multimeter measurement is inapplicable when the number of sheets exceeds  $N = 14$ .

## 4.2 Lock-In Amplifier

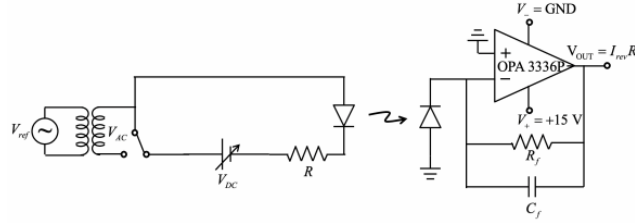


Figure 6: Circuit representation for noise-rich signal modulation in LED circuit

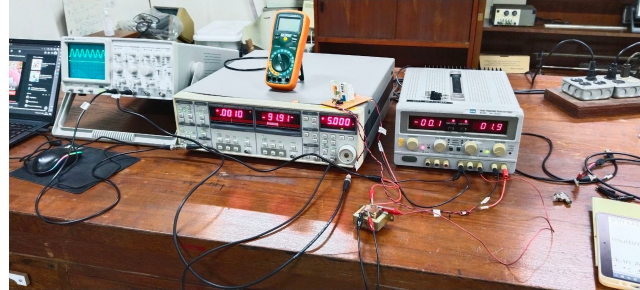


Figure 7: The experimental setup for noise-rich signal modulation in LED circuit

With the setup 7, with a change of output voltage from the multimeter to the Lock-In Amplifier input, the same output voltage can be observed with a different number of sheets. The corresponding output from the Lock-In amplifier to analyze further is  $Y$ .

The graph of  $Y$  and the number of sheets is shown below

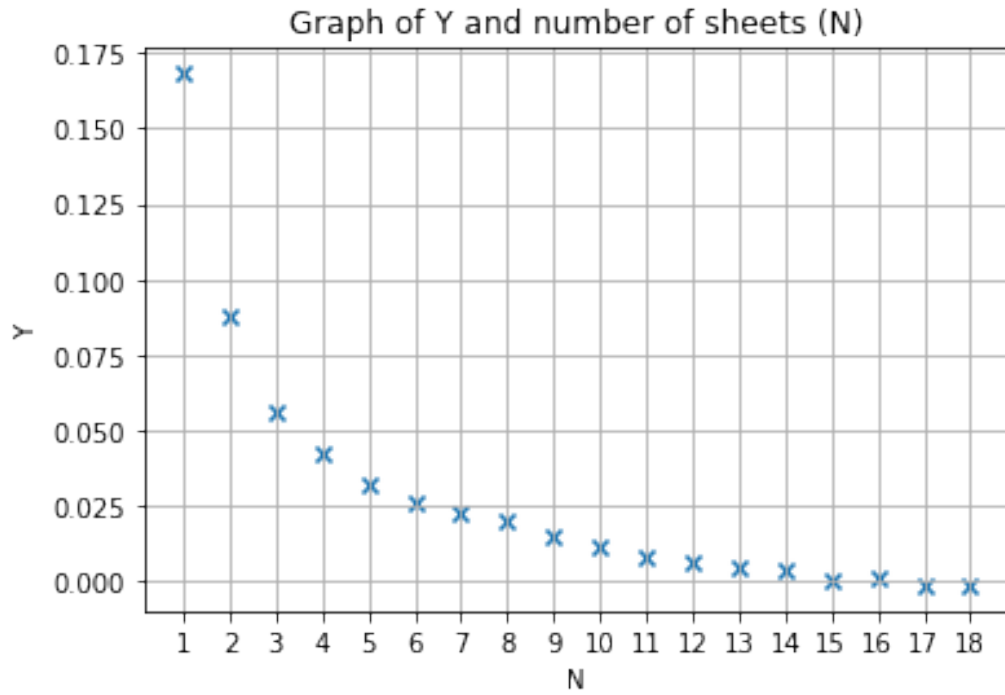


Figure 8: graph of  $Y$  and the number of sheets using the Lock-In Amplifier

From graph 8, the Lock-In Amplifier measurement is inapplicable when the number of sheets exceeds  $N = 16$ .

## 5 Conclusion

The experiment is to use a Lock-In Amplifier in various scenarios. In a resistor-capacitor system, we can obtain the capacitor by using the Lock-In Amplifier  $C = 209 \pm 3$  nF. With measuring a noise-rich signal of an LED circuit, the comparison using a multimeter and a Lock-In Amplifier is conducted. The resulting number of sheets that the voltage measurement is inapplicable from the multimeter is  $N \geq 14$  whereas one from the Lock-In Amplifier is  $N \geq 16$